

Tribhuvan University
Institute of Science and Technology
2069

Bachelor Level/ First Year/ Second Semester/ Science
Computer Science and Information Technology (CSc. 151)
(Digital Logic)

Full Marks: 60
Pass Marks: 24
Time: 3 hours.

Candidates are required to give their answers in their own words as far as practicable. The figures in the margin indicate full marks.

Long Answer Questions:
Attempt any two questions.

(2x10=20)

1. What is a decoder? Implement the following using decoder.
 - a) $F(W X Y Z) = \sum (0, 1, 3, 4, 8, 9, 10)$
 - b) $F(W X Y Z) = \sum (1, 3, 5, 6, 11, 13, 14)$
2. What do you mean by asynchronous counter? Design a mod-6 synchronous counter using T Flip-flops.
3. Explain the Master-slave S-R Flip-flop with logic diagram, truth table and timing diagram .

Short Answer Questions:
Attempt any eight questions:

(8x5=40)

4. Design a Half subtractor using only NOR gates.
5. Convert the following decimal numbers into Hexadecimal and Octal number.
 - a) 220
 - b) 1020
6. Design a multiplexer 4 x 1 using only universal gates.
7. What is J – K flip flop? Explain.
8. Write a procedure to reduce K- maps.
9. What are the various types of shift registers?
10. Draw a logic diagram of a 4 bit ripple counter using D- flip flop.
11. Differentiate between combinational logic and sequential logic. List some applications of sequential logic.
12. Explain the decimal adder.
13. Write short notes on:
 - a) Programmable logic array (PLA)
 - b) Triggering at flip-flop
 - c) Memory unit

IOST, TU